

LECTURE 5: CONTINUOUS MODELS

Modeling and Simulation 2
Daniel Georgiev

Winter 2014

POWER SYSTEM DAEs

- Separation of time scales
- Modular Design


AC CIRCUITS

Phasor voltage is related to phasor current by

$$V_{ab} = I_{ab}Z_{ab}$$

Phasor expressions for voltage and current can be used to derive an expression for phasor power.

$$S = P + iQ = VI^*$$

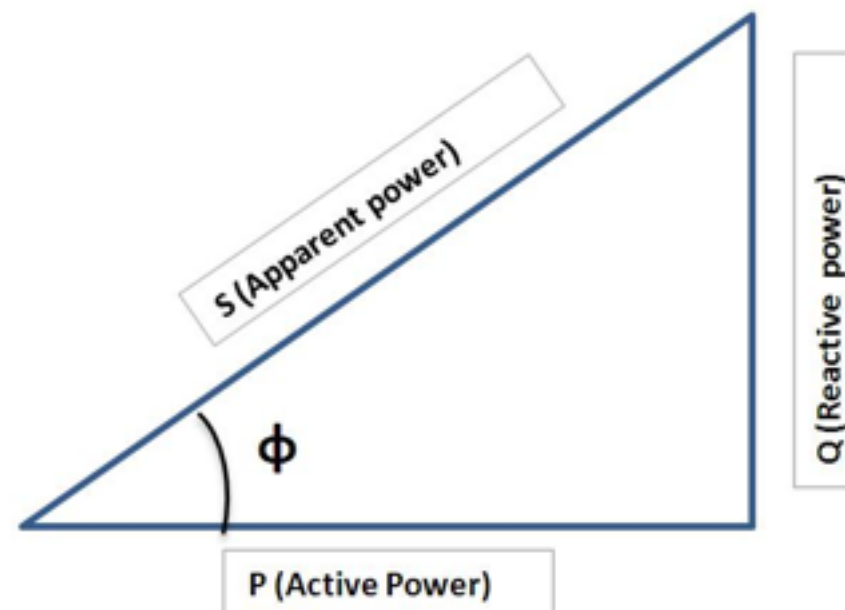

ϕ is the phase angle
The cosine of ϕ gives the Power factor

PER UNIT NOTATION

Power transmission lines are operated at voltage levels in the ranges of kV.

For convenience, quantities are often expressed as “per unit” of a base value.

Kirchhoff's current and voltage laws applied in per unit scale return per unit quantities.

$$\text{Base current, A} = \frac{\text{base, kVA}}{\text{base voltage, kV}}$$


$$\text{Base impedance, } \Omega = \frac{\text{base voltage, V}}{\text{base current, A}}$$

$$\text{Per-unit impedance/voltage/current} = \frac{\text{actual impedance/voltage/current}}{\text{base impedance/voltage/current}}$$

TRANSFORMERS

Assumptions:

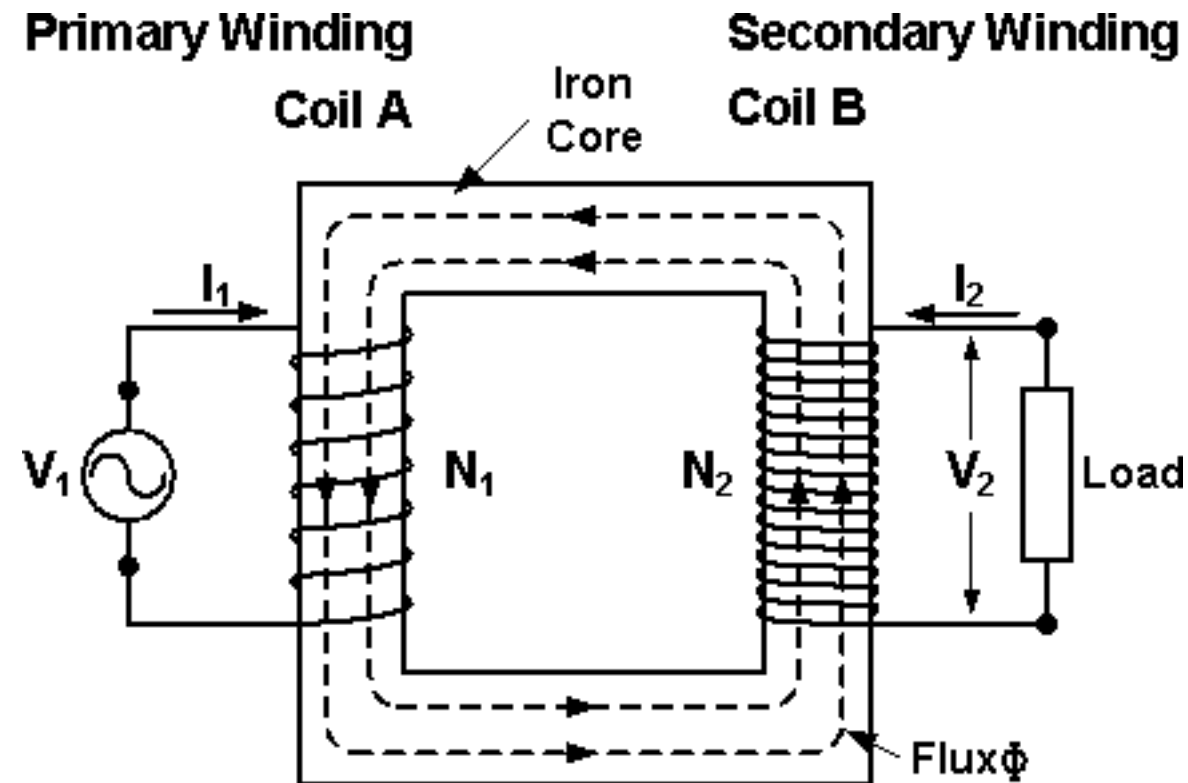- 1) permeability is infinite
- 2) no flux leaked
- 3) no winding resistance
- 4) no losses in iron core



$$v_1 = e_1 = N_1 \frac{d\phi}{dt}$$

$$v_2 = e_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{V_1}{V_2} = \frac{E_1}{E_2} = \frac{N_1}{N_2}$$


NETWORK

$$0 = \frac{n}{Z_1}(V_0 - nV_2) - I_S - I_C - \frac{1}{Z_2}(V_2 - V_3)$$


$$0 = S_D - \frac{1}{Z_2}(V_2 - V_3)V_3^*$$

$$\frac{dV_0}{dt} = 0$$


WIND TURBINE

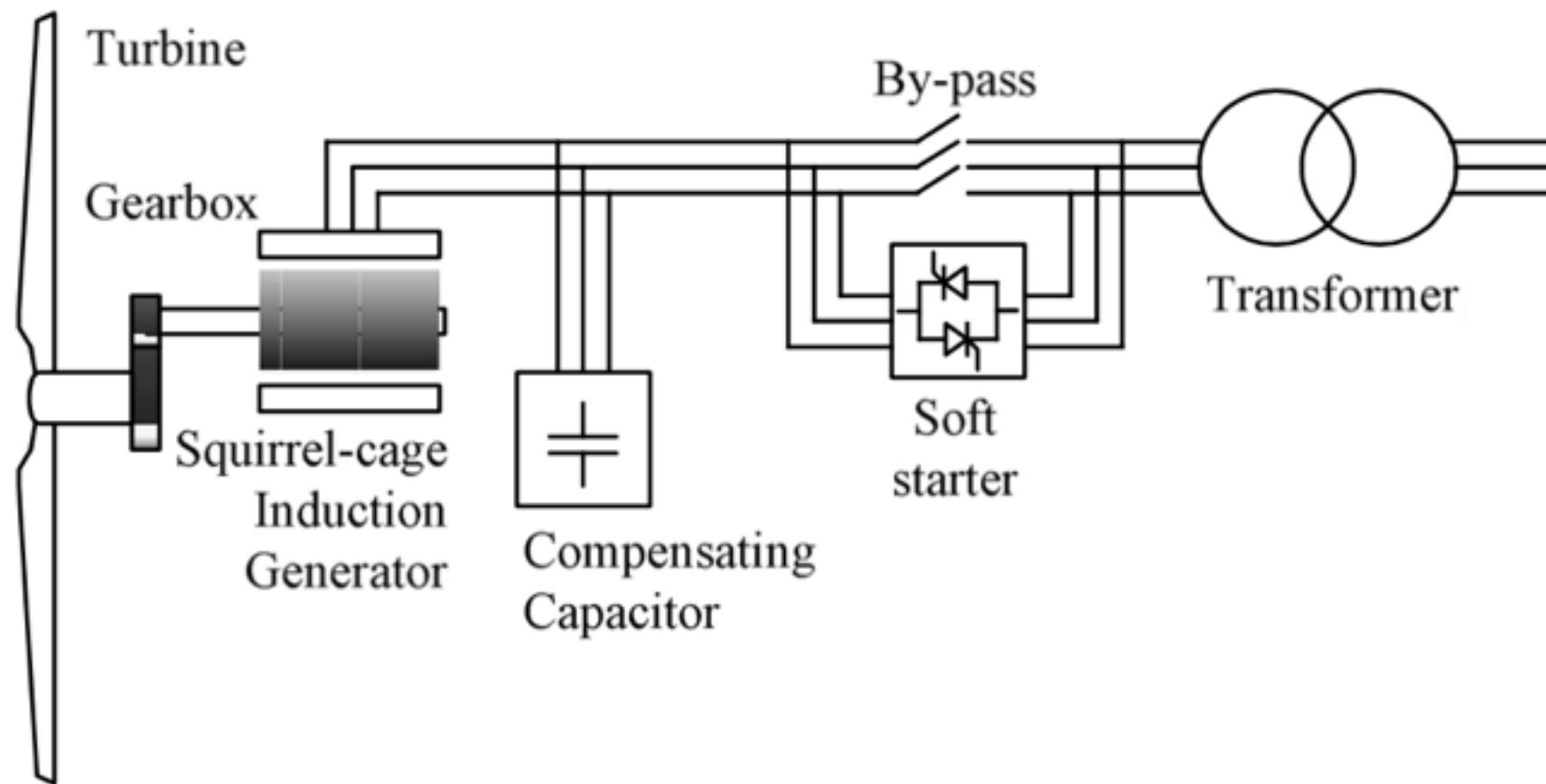

SYNCHRONOUS GENERATOR

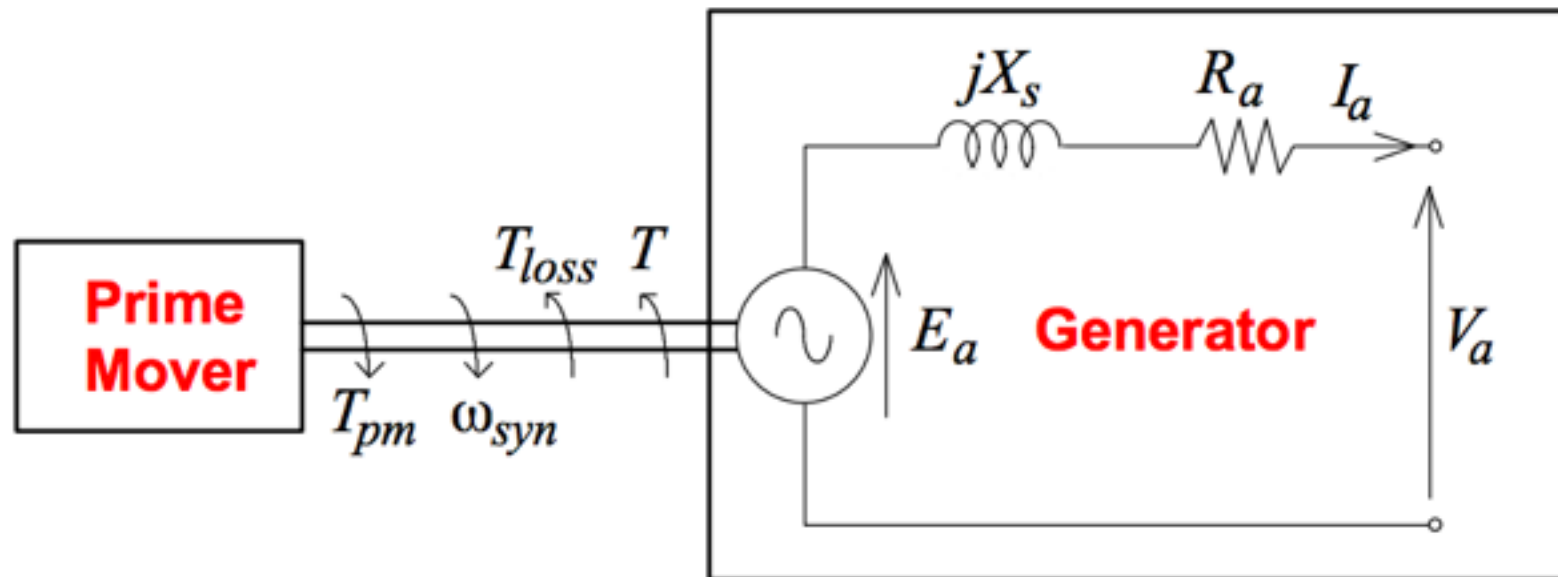

TURBINE

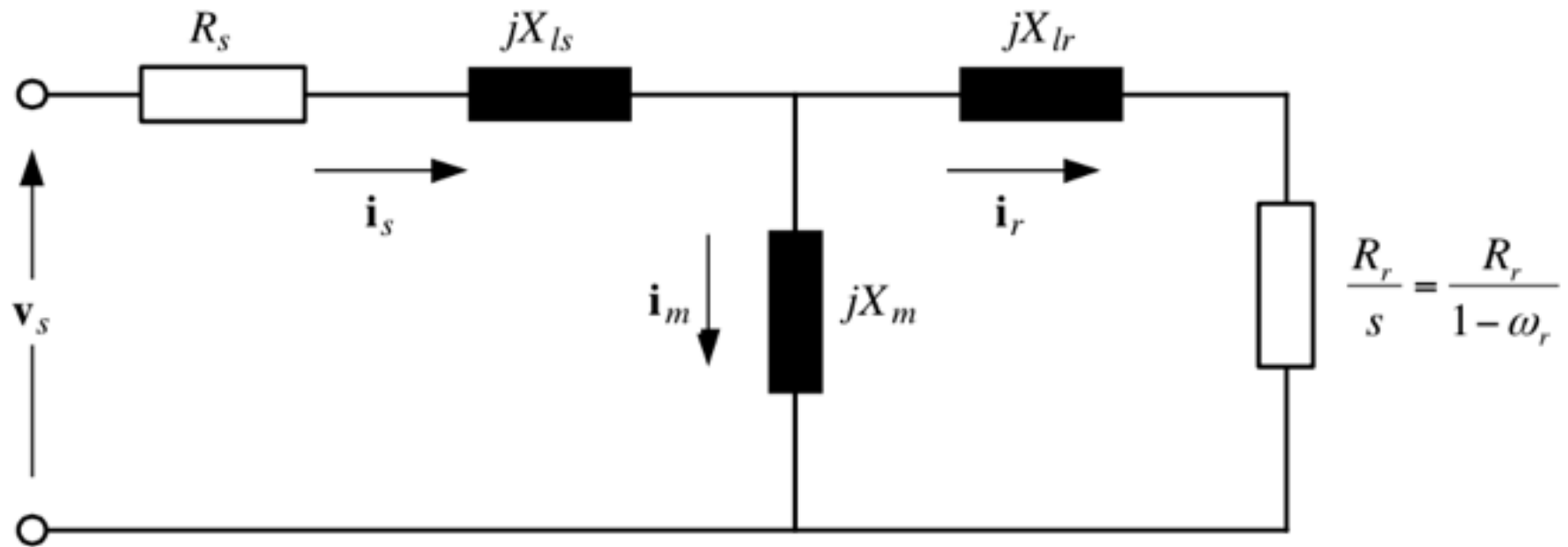

$$0 = -V_2 + I_S(R_S + X_S i) + I_R(X_M i)$$

$$0 = I_S(X_M i) + I_R X_R i - I_R \frac{R_R}{w_R/w_S - 1}$$

$$J_G \dot{w}_R = T_M + \text{Imag}(I_S(I_S X_S/W_S + I_R X_M/W_S)^*)$$

EMPIRICAL MODELS

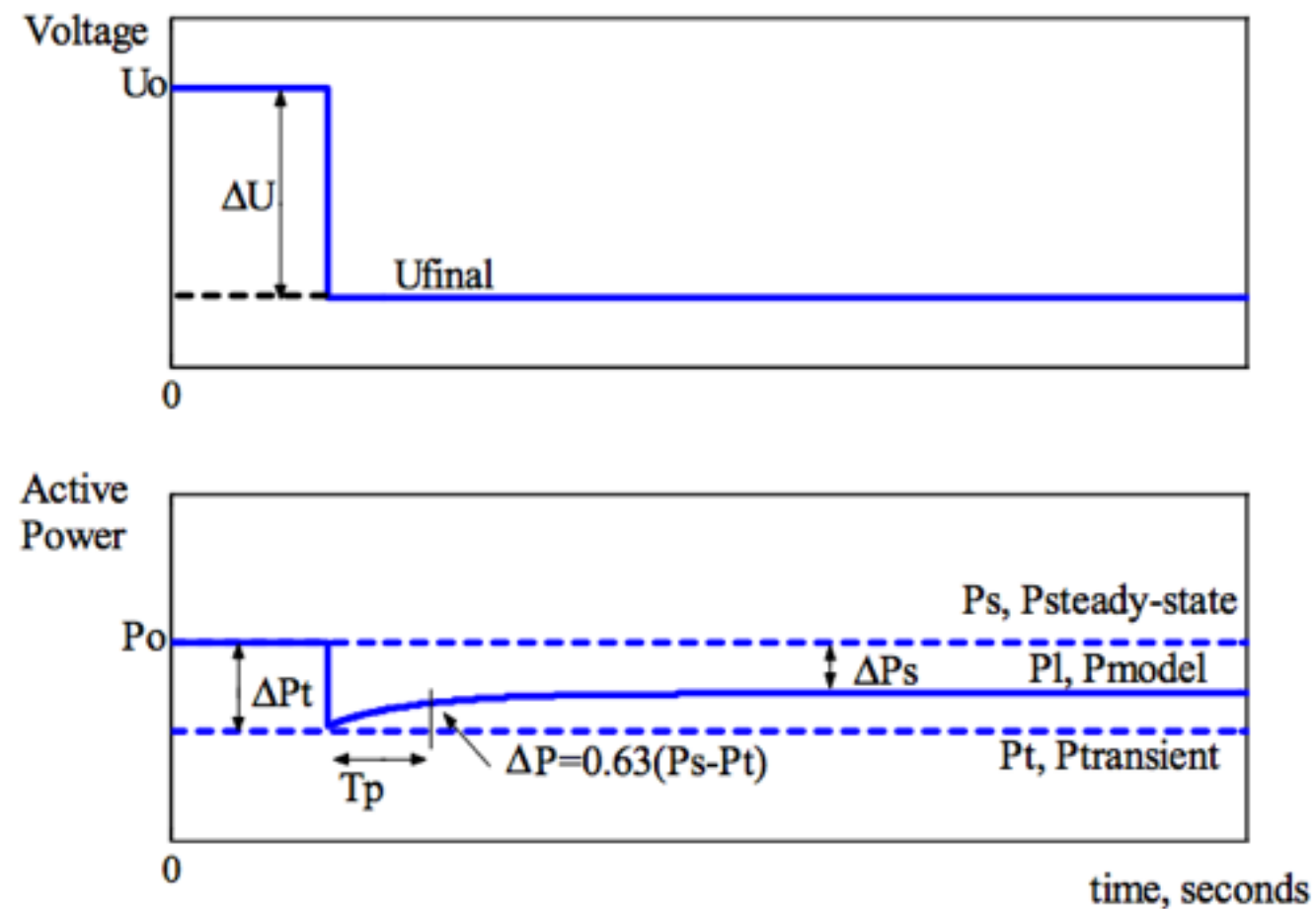


Figure 2.7: Load response under ΔU step, from the U_0 -level.

LOAD

$$\dot{x}_D = -\frac{1}{T_P}(P_D - P_S)$$

$$0 = P_D - x_D - P_T|V_3|_2^2$$

$$0 = Q_D$$

TIMERS

$$\dot{x}_{TC} = onC$$

$$y_{TC} = x_{TC} - tresC$$

$$\dot{x}_{TT} = onT$$

$$y_{TT} = x_{TT} - tresT$$

CAPACITOR BANK

$$0 = I_C - (V_2 C n_C) i$$

LOAD FLOW PROBLEM

Real power balance is given by the equation

$$P_i = \sum_{k=1}^N |V_i| |V_k| (Y_{ik}^R \cos \theta_{ik} + Y_{ik}^I \sin \theta_{ik})$$

Reactive power balance is given by the equation

$$Q_i = \sum_{k=1}^N |V_i| |V_k| (Y_{ik}^R \sin \theta_{ik} - Y_{ik}^I \cos \theta_{ik})$$

Many network problems require the calculation of voltages and currents given the real and reactive powers. This problem is usually solved using the Newton-Raphson method. The following steps are repeated until convergence is reached.

- 0) Set all voltage magnitudes to 1.0 p.u. and angles to zero and all voltage magnitudes are set to 1.0 p.u.
- 1) Solve the power balance equations using the most recent magnitude and angle values $\rightarrow \Delta P, \Delta Q$
- 2) Linearize the system around the most recent magnitude and angle values $\rightarrow \frac{\partial(P,Q)}{\partial(|V|,\theta)} = J$
- 3) Solve for the new magnitude and angle values using the mismatch equations.

$$\begin{pmatrix} \Delta |V| \\ \Delta \theta \end{pmatrix} = -J^{-1} \begin{pmatrix} \Delta P \\ \Delta Q \end{pmatrix}$$

- 4) Check the stopping conditions, if met then terminate, else go to step 2.